



1. A first order high pass filter has a cut-off frequency of 1 KHz. An input of 100 Hz is applied with an amplitude of 1V. What will be the output of the filter?
 - (a) 0.1 V
 - (b) 0 V
 - (c) 2.5 V
 - (d) 1 V

2. If an input is activated by a single transition, it is called ...
 - (a) level triggered
 - (b) clock triggered
 - (c) pulse triggered
 - (d) edge triggered

3. In a 8085 microprocessor, which element stores the results of the Arithmetic and Logic Unit (ALU)?
 - (a) Temporary register
 - (b) Accumulator
 - (c) Program counter
 - (d) Address buffer

4. $(A+B)'$ is same as
 - (a) $A \cdot B$
 - (b) $A' \cdot B'$
 - (c) $A' + B'$
 - (d) $A + B$

5. In a BJT, the base current is $2\mu A$. $\beta = 100$. What is the collector current and emitter current respectively?
- (a) $200\mu A, 198\mu A$
 - (b) $100\mu A, 102\mu A$
 - (c) $201\mu A, 200\mu A$
 - (d) $200\mu A, 202\mu A$
6. In which region of the RF spectrum is satellite communication done?
- (a) Terahertz bands (> 100 GHz)
 - (b) Low frequency bands (30 KHz - 300 KHz)
 - (c) High Frequency bands (3 - 30 MHz)
 - (d) Microwave bands (1 - 100 GHz)
7. A down-converter mixer
- (a) Converts RF to RF
 - (b) Converts RF to IF
 - (c) Converts IF to IF
 - (d) Converts IF to RF
8. What is the full form of VCO and PLL?
- (a) Voltage Controlled Oscillator and Phase Locked Loop
 - (b) Voltage Constant Oscillator and Phase Loss Loop
 - (c) Voltage Controlled Oscillator and Phase Loss Loop
 - (d) Voltage Constant Oscillator and Phase Locked Loop
9. If a keyboard with 80 keys needs to be interfaced with a microcontroller, how many bits need to be used to represent all the keys?
- (a) 7 bits
 - (b) 8 bits
 - (c) 6 bits
 - (d) 5 bits

10. A super-heterodyne receiver is designed to receive a 1 GHz signal. The local oscillator frequency is 900 MHz. What is the image frequency that should be rejected?
- (a) 900 MHz
 - (b) 1.1 GHz
 - (c) 800 MHz
 - (d) 2 GHz
11. If 3 amps flows through a 1 ohm resistor, what is the voltage dropped?
- (a) $1/3$ V
 - (b) $1/9$ V
 - (c) 3 V
 - (d) 9 V
12. How many bits input does a K-map for full adder have?
- (a) 3
 - (b) 4
 - (c) 2
 - (d) 8
13. A 300 V voltmeter has 2% full scale error. If the voltmeter reads 200 V, the actual voltage lies between ...
- (a) exactly 200 V
 - (b) 196 V - 204 V
 - (c) 194 V - 206 V
 - (d) 198 V to 202 V
14. Convert 1001 1000 1011 1010 1100 0101 into hexa-decimal number.
- (a) 98BAC5
 - (b) 88BAC5
 - (c) A8BAC5
 - (d) 98CAB5

15. A circuit consists of a comparator, where one of the input terminals is connected to a rail-to-rail triangle wave and the other is connected to the input signal. What type of modulation do you get at the output of the comparator?
- (a) Pulse Position Modulation
 - (b) Pulse Code Modulation
 - (c) Delta Modulation
 - (d) Pulse Width Modulation
16. Choose the most accurate voltmeter.
- (a) 100 V, 0.2 A
 - (b) 100 V, 20 mA
 - (c) 100 V, 10 mA
 - (d) 100 V, 0.1 A
17. What is the element used in spike buster?
- (a) Varactor
 - (b) Resistor
 - (c) Inductor
 - (d) Varistor
18. If an inductive load is fed from a square wave voltage, which of the following is true?
- (a) The fundamental component is in phase with respect to the applied voltage.
 - (b) The fifth harmonic current amplitude is 1/25th of the fundamental current amplitude.
 - (c) The current through the inductor is sinusoidal.
 - (d) The current through the inductor is a square wave.
19. Which of the following memories does not get erased when powered off?
- (a) Cache
 - (b) DRAM
 - (c) SRAM
 - (d) ROM


20. A receiver consists of an envelope detector and comparator. What type of digital modulation can it handle?

- (a) ASK/OOK
- (b) FSK
- (c) PSK
- (d) None of the above

21. A ground station transmits 500W power. The loss is measured to be 120 dB. What is the received power at the satellite?

- (a) 500 pW
- (b) 500 μ W
- (c) 500 fW
- (d) 500 nW

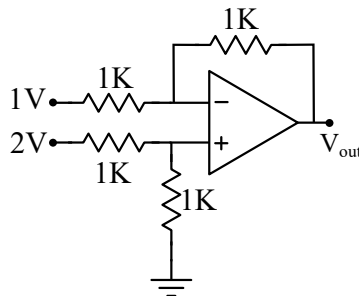22. What is the output voltage of following circuit?




- (a) 3 V
- (b) 2 V
- (c) 0.5 V
- (d) 1 V

23. In which layer of the TCP/IP protocol is the IP addresses handled?

- (a) Host-to-Host/Transport layer
- (b) Network access/Link layer
- (c) Internet layer
- (d) Process/Application layer


24. One unit of electrical energy is equivalent to ...
- (a) 1 KJ
 - (b) 1 kWh
 - (c) 1 hp
 - (d) 1 Wh
25. What is the job of a compiler in a microcontroller programming?
- (a) Translates a high-level language program to machine language
 - (b) Translates a high-level language program to assembly language
 - (c) Translates a assembly language program to machine language
 - (d) Translates a machine language program to assembly language
26. Which of the following statements is true regarding 3-phase power measurement by two watt-meter method?
- (a) Measurement can only be made for star connected loads.
 - (b) If both the meters read equal and opposite values, the power factor is zero.
 - (c) The sum of the values shown is $2/3$ of the total power.
 - (d) Measurement can only be made for delta connected loads.
27. Which of the following statements is true for an opamp?
- (a) Opamp has low input resistance
 - (b) Gain of an opamp is zero
 - (c) Opamp has high input resistance
 - (d) Opamp has high output resistance

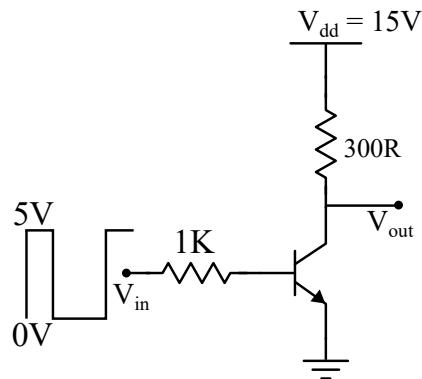28. What is the output of the following circuit?



- (a) Toggles between 0V to 15V, inverting
- (b) Toggles between 0V to 5V, non-inverting
- (c) Toggles between 0V to 15V, non-inverting
- (d) Toggles between 0V to 5V, inverting

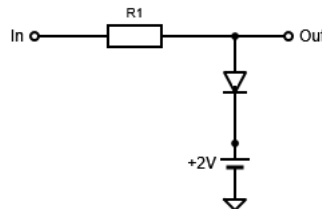29. Consider the circuit shown below. The input is a sinewave of 5V amplitude. What will the output be?



Assume the diode drop to be 0.

- (a) Full sinewave of 2V amplitude
- (b) Full sinewave of 5V amplitude
- (c) Sinewave clipped at -2V
- (d) Sinewave clipped at +2V


30. If two resistors of value $100\ \Omega \pm 1\%$ is connected in series, the total resistance is ...

- (a) $200 \pm 1\%$
- (b) $100 \pm 1\%$
- (c) $100 \pm 2\%$
- (d) $200 \pm 2\%$

31. In a 555 timer, the three $5\text{ k}\Omega$ resistors provide a trigger level of

- (a) $1/2V_{cc}$ and a threshold voltage of $2/3V_{cc}$
- (b) $2/3V_{cc}$ and a threshold voltage of $1/3V_{cc}$
- (c) $1/3V_{cc}$ and a threshold voltage of $1/2V_{cc}$
- (d) $1/3V_{cc}$ and a threshold voltage of $2/3V_{cc}$

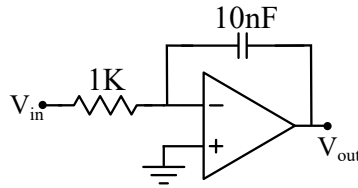32. What is the operation of the following circuit?



- (a) high pass filter
- (b) integrator
- (c) summer
- (d) differentiator

33. The input-output relationship for an inverting amplifier is ...
 R_f is feedback resistor, R_{in} is the input resistor.

- (a) $V_o = -\frac{R_f}{R_{in}}V_{in}$
- (b) $V_o = \frac{R_{in}}{R_f}V_{in}$
- (c) $V_o = -\frac{-R_f}{R_{in}}V_{in}$
- (d) $V_o = -\frac{-R_{in}}{R_f}V_{in}$

34. What should be the sequence of elements in a receiver?

- (a) Mixer, low noise amplifier, low pass filter, band pass filter
- (b) Low noise amplifier, low pass filter, mixer, bandpass filter
- (c) Band pass filter, mixer, low noise amplifier, low pass filter
- (d) Band pass filter, low noise amplifier, mixer, Low pass filter


35. In which of the configurations of the BJT, does the gain always remain slightly less than unity?

- (a) Common Collector
- (b) Common Emitter
- (c) Common Base
- (d) None of the above

36. The 8051 microcontroller is used in 16-bit timer mode. If the clock frequency is 100 KHz, and the timer starts from 0x0000, what will be the timer value in decimal, when it reaches 100 milliseconds?

- (a) 100000
- (b) 10000
- (c) 1000
- (d) 1000000

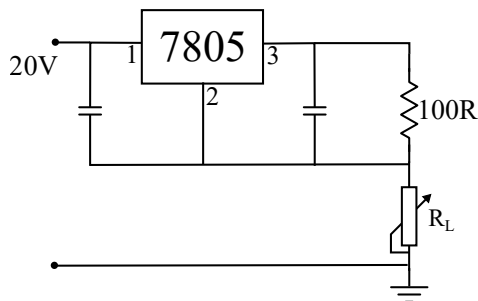37. What is the current through resistor R_L ?



- (a) 50 mA
- (b) 5 mA
- (c) 500 mA
- (d) 1.5 A

38. In a programmable keyboard controller, interfaced to a microcontroller, which of the following describes the interrupt mode of interface?
- (a) The CPU checks periodically, but it also gets interrupted when a key is pressed.
 - (b) The CPU periodically reads an internal flag of the controller to check whether any key is pressed or not.
 - (c) The processor is requested service only if any key is pressed, otherwise the CPU will continue with its main task.
 - (d) None of the above
39. What are the states in a tristate buffer?
- (a) HIGH and LOW
 - (b) HIGH, LOW and low impedance
 - (c) HIGH, LOW and high impedance
 - (d) HIGH, LOW and short
40. A circuit is required to produce a square wave of time period $500\mu s$. Which of the following circuits should be used?
- (a) Bistable multivibrator
 - (b) Comparator
 - (c) Astable multivibrator
 - (d) Monostable multivibrator
41. What is the BCD code for the number $(21)_{10}$?
- (a) 10101
 - (b) 11001
 - (c) 10001
 - (d) 10111
42. The function of shunt resistance in an ammeter is ...
- (a) to increase sensitivity
 - (b) to bypass current
 - (c) to decrease range
 - (d) to drop voltage

43. If a 10-bit ADC is used to sense voltage between 0 to 3 V, what is the resolution of the ADC?
- (a) $2.92 \mu\text{V}$
 - (b) 2.92 mV
 - (c) 1 bit
 - (d) 300 mV
44. If resistance has to be measured by voltmeter-ammeter method, the voltmeter can be connected across the source, or the resistance. If the resistance is low, the voltmeter should be connected ...
- (a) preferably across source
 - (b) across the source
 - (c) in any position
 - (d) across the resistor
45. What happens inside an optocoupler?
- (a) Optical to electrical conversion followed by electrical to optical conversion
 - (b) Optical to magnetic conversion followed by magnetic to optical conversion
 - (c) Optical to optical conversion
 - (d) Electrical to optical conversion followed by optical to electrical conversion
46. If the SOP form of a look-up-table is given as $\sum A, B, C(1, 3, 6, 7)$, the expression is equal to
- (a) $(A'C+AB)$
 - (b) $(AC+B'C)$
 - (c) $(CB+B'C')$
 - (d) $(AC+BC')$
47. A transmitter consists of an oscillator in which the input signal (message signal) is fed to a varactor. What type of modulation will be produced?
- (a) Amplitude modulation
 - (b) Pulse width modulation
 - (c) Frequency modulation
 - (d) None of the above

48. A network topology in which the nodes are so connected that at least some or all have multiple paths to other nodes is called as

- (a) Star
- (b) Mesh
- (c) Ring
- (d) None of the above

49. The BCD number of 1001 1010 1011 has ...

- (a) no parity
- (b) odd parity
- (c) parity can not be determined
- (d) even parity

50. A full bridge inverter is fed from a DC supply of voltage V_{dc} and is switching in square wave mode. What is the peak fundamental voltage generated at the output?

- (a) $\frac{4V_{dc}}{\pi}$
- (b) V_{dc}
- (c) $V_{dc}/2$
- (d) $\frac{2V_{dc}}{\pi}$

51. The statement "JC 2055" in a 8085 microprocessor program means

- (a) Jump to address location 2055 unconditionally
- (b) Jump to address location if there is negative number
- (c) Jump to address location 2055 if there is a carry
- (d) Jump to address location 2055 if there is no carry

52. A square wave of amplitude 1, with 50% duty cycle and period 2π can be represented as ...


- (a) $\frac{4}{\pi} \sum_{n=1,2,3...} \frac{\sin(nt)}{n}$
- (b) $\frac{2}{\pi} \sum_{n=1,3,5...} \frac{\sin(nt)}{n}$
- (c) $\frac{2}{\pi} \sum_{n=1,2,3...} \frac{\sin(nt)}{n}$
- (d) $\frac{4}{\pi} \sum_{n=1,3,5...} \frac{\sin(nt)}{n}$

53. In TTL logic, the typical output voltage range for HIGH logic is
- (a) 2.25 V to 2.75 V
 - (b) 4.75 V to 5.25 V
 - (c) 3.0 V to 3.6 V
 - (d) 1.7 V to 1.9 V
54. A 12-bit clock divider is used to divide a 50 MHz clock. What is the frequency of the synthesized clock?
- (a) 4.16 MHz
 - (b) 48.83 kHz
 - (c) 12.20 kHz
 - (d) 24.41 kHz
55. What is the guaranteed level of output voltage for '0' state?
- (a) V_{OL}
 - (b) V_{OH}
 - (c) V_{IH}
 - (d) V_{IL}
56. What are the anomalies in a power supply line that a voltage stabilizer can correct?
- (a) Voltage fluctuations
 - (b) Cycle changes
 - (c) Voltage spikes
 - (d) Power failures
57. Which of the following converters is an isolated converter?
- (a) Forward converter
 - (b) Buck converter
 - (c) SEPIC converter
 - (d) Cuk converter

58. If a temperature sensor takes 10 seconds to stabilize, how much time would be required to reach half the value between the initial and final reading?
- (a) 5 sec.
 - (b) 8 sec.
 - (c) 1.38 sec.
 - (d) 6.32 sec.
59. A step-down chopper is connected to 125 V supply. If the chopper is operated at 50% duty cycle and the load consumes 100 watts of power, what is the input current? Assume the converter efficiency is 80%
- (a) 1.667 A
 - (b) 150 A
 - (c) 1 A
 - (d) 0.833 A
60. What is the correct order in a instruction cycle?
- (a) Read address from memory - fetch instruction - decode - execute
 - (b) Fetch instruction - decode - Read address from memory - execute
 - (c) Execute - read address from memory - fetch instruction - decode
 - (d) Fetch instruction - Read address from memory - decode - execute
61. Which type of opamp should be used for low current measurements?
- (a) Instrumentation amplifier
 - (b) Differential Opamp
 - (c) Comparator Opamp
 - (d) Electrometer opamp
62. If a semiconductor switch has a conduction loss of 100 mW in a circuit for an average current of 1 A, what would be the conduction loss for an average current of 2 A if the voltage drop across the device is constant irrespective of the switch current?
- (a) 200 mW
 - (b) 400 mW
 - (c) 50 mW
 - (d) 100 mW

63. The 8086 microprocessor has a 20-bit address line. How many memory locations can it access?
- (a) 2097152
 - (b) 2048
 - (c) 1048576
 - (d) 20
64. A signal with a bandwidth of 40 KHz is to be digitized. Of the following sampling rates available, which one should be chosen?
- (a) 40 KHz
 - (b) 78 KHz
 - (c) 100 KHz
 - (d) 50 KHz
65. In a GPS system, which of the following is true?
- (a) It is a two-way communication between satellites and GPS units
 - (b) It is a one-way communication from GPS unit to satellites
 - (c) It is one-way communication from satellites to GPS unit
 - (d) None of the above
66. In a CRO, the output frequency of the time base signal is ...
- (a) a fixed signal
 - (b) a random signal
 - (c) an adjustable signal
 - (d) proportional to sensed voltage

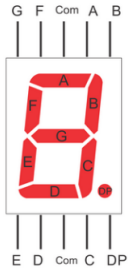67. The seven-segment display as shown below needs programming in a common-cathode style (Bit to be high for the LED to glow). What is the code to represent 7 without the dot in the order (DP)GFEDCBA?



- (a) 0x07
 - (b) 0x0D
 - (c) 0x0F
 - (d) 0x0B
68. How many flip-flops are required to produce a divide-by-128 device?
- (a) 127
 - (b) 128
 - (c) 7
 - (d) 9
69. Which of the following is true about a stored program concept?
- (a) Only the data is stored in the computer memory
 - (b) Both instructions and data are stored in the computer memory
 - (c) Only the instructions are stored in the computer memory
 - (d) Only the results are stored in the computer memory
70. What is the function of "Program Counter" in a 8085 microprocessor?
- (a) Holds the address of the output of the previous execution
 - (b) Holds the address of the next instruction to be executed
 - (c) Holds the address of the previous instruction executed
 - (d) Holds the address of the next data to be processed

71. How should a Zener diode be biased if it has to act as a voltage regulator?

- (a) Short circuited
- (b) Forward biased
- (c) Disconnect one of the terminals
- (d) Reverse biased

72. What is the input-output relationship of a boost converter?

- (a) $V_o = V_{in} \cdot D$
- (b) $V_o = V_{in}/(1 - D)$
- (c) $V_o = V_{in} \cdot D/(1 - D)$
- (d) $V_o = V_{in}/D$

73. Why do we need relays to switch motors or lights?

- (a) The microcontroller cannot switch such high current loads by itself
- (b) To reduce processing time
- (c) To give more flexibility
- (d) To increase the speed of switching

74. In a doped semiconductor, if the dopant introduces excess electrons, what type is it?

- (a) Intrinsic
- (b) Conductor
- (c) P-type
- (d) N-type

75. Which flip-flop will be synthesized by the following VHDL code?

```
process(clk)
if(clk'event and clk=1)
output <= input;
end if;
end process;
```

- (a) T flip-flop
- (b) SR flip-flop
- (c) D flip-flop
- (d) JK flip-flop

76. A 1 kW linear regulator is used to obtain 12 V from 20 V unregulated supply. Its nominal efficiency at full load and no load operation respectively is ...

- (a) 0.6, 0.4
- (b) 0.4, 0.6
- (c) 0.6, 0.6
- (d) 0.4, 0.4


77. A full bridge inverter is fed from a 325 V DC supply. If the modulation index of the inverter is 0.5, and if sine triangle modulation technique is used, what is the RMS value of the fundamental component of the output voltage?

- (a) 325×2
- (b) $\frac{325 \times 0.5}{\sqrt{2}}$
- (c) $325\sqrt{2}$
- (d) $\frac{325 \times 0.5}{2\sqrt{2}}$

78. The difference between a CALL statement and JMP statement is

- (a) None of the above
- (b) CALL pushes the address of the instruction that would have come next into the stack before branching.
- (c) There is no difference between the two
- (d) JMP pushes the address of the instruction that would have come next into the stack before branching.

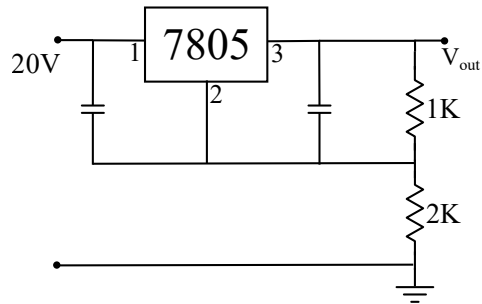79. What is the output voltage of the following circuit?



- (a) 10 V
- (b) 15 V
- (c) 20 V
- (d) 5 V

80. Which of the following is the normal way to turn on a SCR?

- (a) Increasing voltage beyond blocking voltage
- (b) Injecting anode current
- (c) Injecting gate current
- (d) Injecting cathode current

81. In the instruction MOV AL, 34h, which is the opcode?

- (a) AL
- (b) MOV
- (c) 34h
- (d) None of the above

82. What are the application of a PIN diode?

- (a) Variable resistor
- (b) RF switches
- (c) High voltage rectifier
- (d) All the above

83. When communication happens in only one direction all the time, then it is in
- (a) Half duplex mode
 - (b) Full duplex mode
 - (c) Simplex mode
 - (d) None of the above
84. AM modulation is performed on a 5 MHz carrier. The message signal has a bandwidth of 2 KHz. What is the bandwidth of the modulated signal?
- (a) 4 KHz
 - (b) 2 KHz
 - (c) 5 MHz
 - (d) 5.2 MHz
85. A meter has a square law scale. For 2 A current, the deflection is 90° . What would be the current if deflection is 45° ?
- (a) 1.414 A
 - (b) 1.0 A
 - (c) 1.5 A
 - (d) 0.707 A
86. Which of the following memories is the slowest in a computer?
- (a) Hard disk
 - (b) RAM
 - (c) EEPROM
 - (d) Cache
87. In free space propagation, as distance 'd' from the transmitter increases, the received power reduces by ...
- (a) a factor of d^3
 - (b) a factor of d
 - (c) a factor of $d^{0.5}$
 - (d) a factor of d^2

88. How does a queue work?

- (a) First in - first out
- (b) Last in - first out
- (c) First in - last out
- (d) None of the above

89. Which circuit is the best way to convert 3.3V logic into a 5V logic?

- (a) Buffer
- (b) Non-inverting voltage amplifier
- (c) Comparator with pull-up resistor
- (d) Inverting voltage amplifier

90. A 10mW signal is fed to an attenuator of 6 dB. What is the output power?

- (a) 5 mW
- (b) 1.25 mW
- (c) 2.5 mW
- (d) 7.5mW